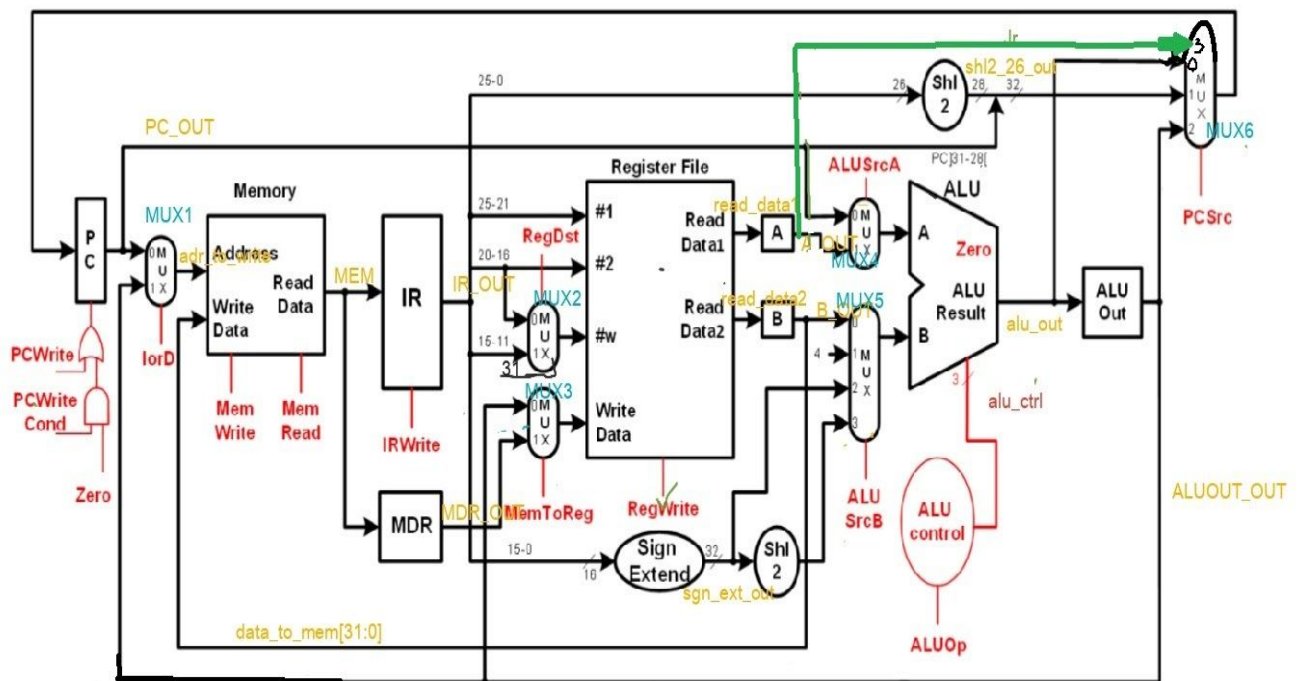


Computer Assignment #3 (Multi Cycle MIPS Processor)

Helia Hosseini (810197491)
Daneshvar Amrollahi (810197685)

Datapath:

Block Diagram:



Verilog Code:

```
module datapath (clk,
                rst,
                mem,
                data_to_mem,
                reg_dst,
                mem_to_reg,
                alu_src_a,
                alu_src_b,
                pc_src,
                alu_ctrl,
                reg_write,
                zero_out,
                zero_in,
                adr_to_write,
                IorD,
                pc_write,
                pc_write_cond,
                ir_write,
                inst);

    input  clk, rst;
    output [31:0] data_to_mem;
    input  [31:0] mem;
    input  [1:0] reg_dst;
    input  mem_to_reg, alu_src_a, reg_write, ir_write, IorD, pc_write,
pc_write_cond, zero_in, zero_out;
    input  [1:0] alu_src_b;
    input  [1:0] pc_src;
    input  [2:0] alu_ctrl;
    output [31:0] adr_to_write;
    output [31:0] inst;

    wire [31:0] pc_out;
    wire [31:0] read_data1, read_data2;
    wire [31:0] sgn_ext_out;
    wire [4:0] mux2_out;
    wire [31:0] alu_out;
    wire [31:0] sh12_32_out;
    wire [31:0] mux3_out;
    wire [31:0] mux4_out;
    wire [31:0] mux1_out;
```

```

wire [31:0] mux5_out;
wire [27:0] sh12_26_out;
wire [31:0] mux6_out;
wire [31:0] ir_out;
wire [31:0] mdr_out;
wire [31:0] a_out;
wire [31:0] b_out;

wire [31:0] aluout_out;

reg_32b PC(mux6_out, rst, (zero_in & pc_write_cond) | pc_write, clk,
pc_out);

mux2to1_32b MUX1(pc_out, aluout_out, IorD, mux1_out);

reg_32b IR(mem, rst, ir_write, clk, ir_out);

reg_32b MDR(mem, rst, 1'b1, clk, mdr_out);

mux3to1_5b MUX2(ir_out[20:16], ir_out[15:11], 5'b11111, reg_dst, mux2_out);

mux2to1_32b MUX3(aluout_out, mdr_out, mem_to_reg, mux3_out);

reg_file RF(mux3_out, ir_out[25:21], ir_out[20:16], mux2_out, reg_write,
rst, clk, read_data1, read_data2);

sign_ext SGN_EXT(ir_out[15:0], sgn_ext_out);
sh12_32b SHL2_32B(sgn_ext_out, sh12_32_out);

reg_32b A(read_data1, rst, 1'b1, clk, a_out);
reg_32b B(read_data2, rst, 1'b1, clk, b_out);

mux2to1_32b MUX4(pc_out, a_out, alu_src_a, mux4_out);

mux4to1_32b MUX5(b_out, 32'd4, sgn_ext_out, sh12_32_out, alu_src_b,
mux5_out);

alu ALU(mux4_out, mux5_out, alu_ctrl, alu_out, zero_out);

sh12_26b SHL2_26B(ir_out[25:0], sh12_26_out);

reg_32b ALUOUT(alu_out, rst, 1'b1, clk, aluout_out);

mux4to1_32b MUX6(alu_out, {pc_out[31:28], sh12_26_out}, aluout_out, a_out,

```

```
pc_src, mux6_out);  
  
    assign adr_to_write = mux1_out;  
  
    assign data_to_mem = b_out;  
  
    assign inst = ir_out;  
endmodule
```

Instruction Formats:

Set Less Than Immediate:

```
SLTi Rt Rs data
```

Opcode	R _s	R _t	data
001010	[25:21]	[20:16]	[15:0]

Jump and Link:

```
Jal adr
```

Opcode	adr
000011	[25:0]

Jump Register:

```
Jr Rs
```

Opcode	R _s	X
000110	[25:21]	X


Jump:





```
J adr
```

Opcode	adr
000010	[25:0]

Controller:

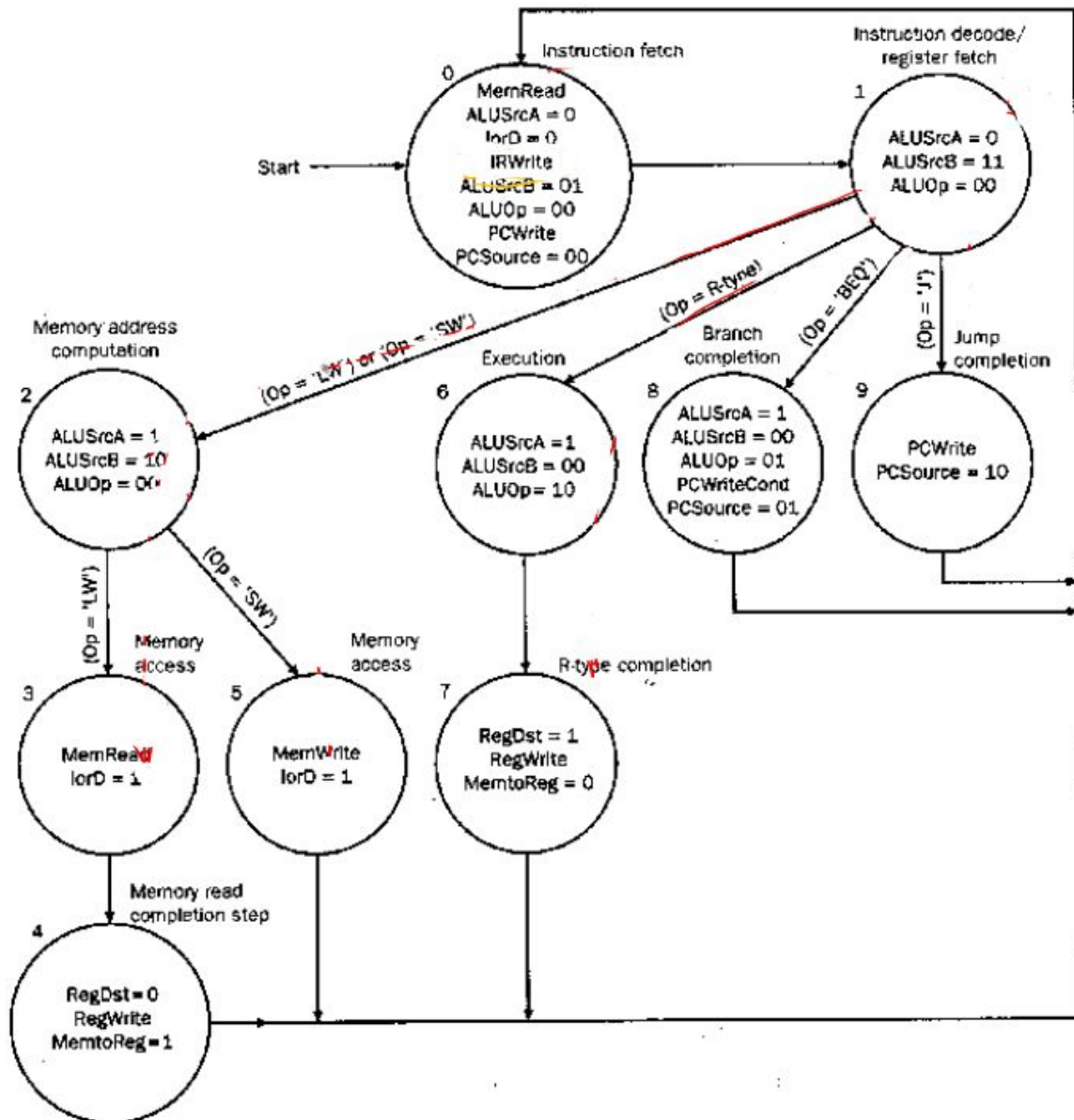The controller can be shown as the union of FSMs below:



  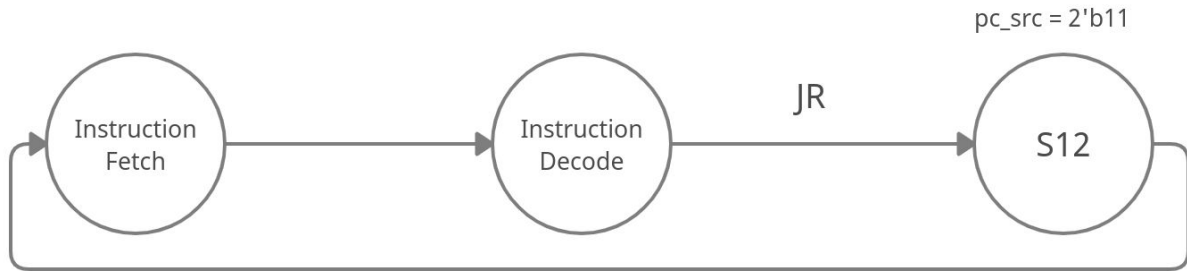 

Verilog Code:

The controller is implemented using huffman coding style:

```
`define S0      5'b00000
`define S1      5'b00001
`define S2      5'b00010
`define S3      5'b00011
`define S4      5'b00100
`define S5      5'b00101
`define S6      5'b00110
`define S7      5'b00111
`define S8      5'b01000
`define S9      5'b01001
`define S10     5'b01010
`define S11     5'b01011
`define S12     5'b01100
`define S13     5'b01101
`define S14     5'b01110
`define S15     5'b01111
`define S16     5'b10000
```

```
`define J       6'b000010
`define JAL     6'b000011
`define SLTI    6'b001010
`define JR      6'b000110
`define ADDI    6'b001001
`define BEQ     6'b000100
`define RTYPE   6'b000000
`define LW      6'b100011
`define SW      6'b101011
```

```
module controller (opcode,
                  func,
                  zero_out,
                  zero_in,
                  reg_dst,
                  mem_to_reg,
                  reg_write,
                  mem_read,
                  mem_write,
                  pc_src,
```



```

        operation,
        pc_write,
        pc_write_cond,
        IorD,
        ir_write,
        alu_src_a,
        alu_src_b,
        clk,
        rst);

output zero_out;
input zero_in, clk, rst;
output reg pc_write, pc_write_cond, IorD, ir_write, alu_src_a;
output reg [1:0] alu_src_b;

input [5:0] opcode;
input [5:0] func;
output reg mem_to_reg, reg_write, mem_read, mem_write;
output reg [1:0] pc_src;

output [2:0] operation;

output reg [1:0] reg_dst;

reg [1:0] alu_op;

alu_controller ALU_CTRL(alu_op, func, operation);

reg[4:0] ps, ns;

always @(posedge clk)
begin
    if (rst)
        ps <= `S0;
    else
        ps <= ns;
end

always @(ps, opcode)
begin
    case (ps)
        `S0: ns = `S1;

        `S1: begin
            case(opcode)

```



```

        case (ps)
            `S0:    {mem_read, ir_write, alu_src_b, pc_write} = {1'b1, 1'b1,
2'b01, 1'b1};
            `S1:    {alu_src_b}                                = {2'b11};
            `S2:    {alu_src_a, alu_src_b}                    = {1'b1, 2'b10};
            `S3:    {IorD, mem_read}                          = {1'b1, 1'b1};
            `S4:    {reg_write, mem_to_reg}                    = {1'b1, 1'b1};
            `S5:    {mem_write, IorD}                          = {1'b1, 1'b1};
            `S6:    {alu_src_a, alu_op} = {1'b1, 2'b10};
            `S7:    {reg_dst, reg_write} = {1'b1, 1'b1};
            `S8:    {alu_src_a, alu_op, pc_write_cond, pc_src} = {1'b1, 2'b01,
1'b1, 2'b10};
            `S9:    {pc_write, pc_src} = {1'b1, 2'b01};
            `S10:   {reg_write, reg_dst} = {1'b1, 2'b10};
            `S11:   {pc_src, pc_write} = {2'b01, 1'b1};
            `S12:   {pc_src} = {2'b11}; //Etmaame JR
            `S13:   {alu_src_b, alu_src_a, alu_op} = {2'b10, 1'b1, 2'b11};
            `S14:   {reg_write} = {1'b1};
            `S15:   {alu_src_a, alu_src_b} = {1'b1, 2'b10};
            `S16:   {reg_write} = {1'b1};
        endcase
    end

    assign zero_out = zero_in;

endmodule

```

Testing

The processor is tested using the following test bench:

Load #20 32bit numbers in 2's complement format from a .mem file into Data Memory and find their minimum and it's index and finally store them at address 2000 and 2004 of Data Memory.

Pseudocode:

```
min = a[0]
min_idx = 0

for (int i = 1 ; i < 20 ; i++)
    if (a[i] < mn)
    {
        min = a[i]
        min_idx = i
    }
```

The pseudocode above is converted to an equivalent set of Assembly instructions:

Assembly Instructions:

```
        LW R4, 1000(R0)
        ADDi R5, R0, 0
        ADDi R1, R0, 1
        ADDi R2, R0, 20

iLoop:  Beq R1, R2, AFTER_LOOP
        ADD R3, R0, R1
        ADD R3, R3, R3
        ADD R3, R3, R3
```

```

        LW R7, 1000(R3)
        SLT R6, R7, R4
        Beq R6, R0, END_LOOP
        ADD R4, R0, R7
        ADD R5, R0, R1
END_LOOP: ADDi R1, R1, 1
        J iLoop
AFTER_LOOP: SW R4, 2000(R0)
           SW R5, 2004(R0)

```



The loop variable (i) is stored in R1.
 Minimum value (min) is stored in R4.
 Minimum value's index (min_idx) is stored in R5.

The array of 20 random signed numbers loaded into Data Memory is as followed:

0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19
37	27	49	94	42	28	83	113	62	109	73	82	-41	102	63	111	-27	25	68	32

The first row corresponds to the indices while the second row corresponds to the values stored in that index.

Waveforms:

  

As it can be seen, the minimum number in the test set is $A[12] = -41$ which is shown on *min* and *min_idx* in the waveforms after executing all instructions.