
Computer Assignment #2 (Single Cycle MIPS Processor)

Helia Hoseini (810197491) Daneshvar Amrollahi (810197685)

Datapath:

Block Diagram:

 

Verilog Code

```
reg_32b PC(mux7_out, rst, 1'b1, clk, pc_out);
adder_32b ADDER_1 (pc_out , 32'd4, 1'b0, , adder1_out);
mux3to1 5b MUX 1(inst[20:16], inst[15:11], 5'b11111, reg dst, mux1 out);
mux3to1 32b MUX 5(mux4 out, adder1 out, alu out, data to write, mux5 out);
reg_file RF(mux5_out, inst[25:21], inst[20:16], mux1_out, reg_write, rst,
clk, read_data1, read_data2);
sign_ext SGN_EXT(inst[15:0], sgn_ext_out);
mux2to1_32b MUX_2(read_data2, sgn_ext_out , alu_src, mux2_out);
alu ALU(read_data1, mux2_out, alu_ctrl, alu_out, zero);
shl2 SHL2(sgn_ext_out, shl2_out);
adder_32b ADDER_2(adder1_out, shl2_out, 1'b0, , adder2_out);
mux2to1_32b MUX_3(adder1_out, adder2_out, pc_src, mux3_out);
mux2to1 32b MUX 4(alu out, data in, mem to reg, mux4 out);
shl2_26b SHL26(inst[25:0], shl26_out);
assign in0MUX6 = {adder1_out[31:28], shl26_out};
 mux2to1_32b MUX_6(in0MUX6, read_data1, jr, mux6_out);
mux2to1_32b MUX_7(mux3_out, mux6_out, jmp, mux7_out);
assign inst_adr = pc_out;
assign data adr = alu out; //Address in data memory where data should be
written
assign data out = read data2; //Value that should be written in data memory
```

Instruction Formats

Set Less Than Immediate:

SLTi R_t R_s data

Opcode	R_s	R_{t}	data				
001010	[25:21]	[20:16]	[15:0]				

Jump and Link:

Jal adr

Opcode	adr
000011	[25:0]

Jump Register:

Jr Rs

Opcode	R_s	X
000110	[25:21]	X

Jump:

J adr

Opcode	adr
000010	[25:0]

Controller

Issued signals for components in Datapath for each instruction is shown below:

```
always @(opcode)
   begin
       {reg_dst, alu_src, mem_to_reg, reg_write, mem_read,
mem write, branch, alu op, jmp, jr, data to write} = 14'd0;
       case (opcode)
           // RType instructions
           6'b000000 : {reg dst, reg write, alu op} =
{2'b01, 3'b110};
          // Load Word (lw) instruction
           6'b100011 : {alu src, mem to reg, reg write,
mem_read} = 4'b1111;
           // Store Word (sw) instruction
           6'b101011 : {alu src, mem write} = 2'b11;
           // Branch on equal (beg) instruction
           6'b000100 : {branch, alu op} = 3'b101;
           // Add immediate (addi) instruction
```

```
6'b001001: {reg_write, alu_src} = 2'b11;

// Jump (j) instruction
6'b000010: {jmp} = 1'b1;

// Jump and Link (jal) instruction
6'b000011: {reg_dst, data_to_write, jmp} =
{2'b10, 2'b01, 1'b1};

// Jump Register (JR) instruction
6'b000110: {jr, jmp} = {2'b11};

// Set Less Than immediate (SLTi) instruction
6'b001010: {reg_write, alu_src,
alu_op,data_to_write} = {1'b1, 1'b1, 2'b11, 2'b10};
endcase
end
assign pc_src = branch & z
```

Testing

The processor is tested using the following test bench:

Load #20 32bit numbers in 2's complement format from a .mem file into Data Memory and find their minimum and it's index and finally store them at address 2000 and 2004 of Data Memory.

Pseudocode:

```
min = a[0]
min_idx = 0

for (int i = 1; i < 20; i++)
    if (a[i] < mn)
    {
        min = a[i]
        min_idx = i
    }
}</pre>
```

The pseudocode above is converted to an equivalent set of Assembly instructions:

Assembly Instructions:

```
LW R4, 1000(R0)
ADDi R5, R0, 0
ADDi R1, R0, 1
ADDi R2, R0, 20

iLoop: Beq R1, R2, AFTER_LOOP
ADD R3, R0, R1
ADD R3, R3, R3
ADD R3, R3, R3
```

```
LW R7, 1000(R3)

SLT R6, R7, R4

Beq R6, R0, END_LOOP

ADD R4, R0, R7

ADD R5, R0, R1

END_LOOP: ADDi R1, R1, 1

J iLoop

AFTER_LOOP:SW R4, 2000(R0)

SW R5, 2004(R0)
```

The loop variable (i) is stored in R1.

Minimum value (min) is stored in R4.

Minimum value's index (min_idx) is stored in R5.

The array of 20 random signed numbers loaded into Data Memory is as followed:

0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19
37	27	49	94	42	28	83	113	62	109	73	82	-41	102	63	111	-27	25	68	32

The first row corresponds to the indices while the second row corresponds to the values stored in that index.



As it can be seen, the minimum number in the test set is A[12] = -41 which is shown on min and min_idx in the waveforms after executing all instructions.